

Time: 120 min

Date: 11/03/2025 (FN)



Max. Marks: 40

(4 x 10 = 40)

PART-A

Answer ONE FULL question from each unit

All the Questions Carry EQUAL marks

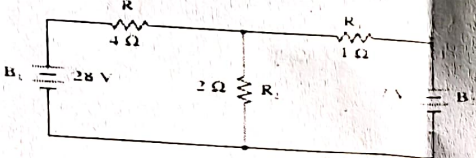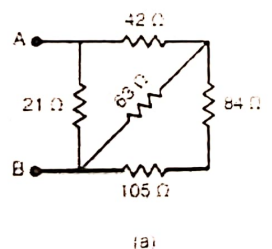Q.No	Question	Unit	BT Level	CO covered	Marks Allotted
1	a) Explain superposition theorem? Verify the superposition theorem for current in 2Ω resistor. 	I	L1	CO1	(8M)
	b) Define ohms law, KVL.	I	L2	CO1	(2M)
(OR)					
2	a) Explain active power, reactive and apparent power.	I	L3	CO1	(8M)
	b) Define Form factor and Peak factor	I	L2	CO1	(2M)
3	a) Explain the working principle of DC machine with a neat diagram	II	L2	CO1	(8M)
	b). What is the working purpose of wheat stone bridge	II	L2	CO1	(2M)
(OR)					
4	a) Explain the working principle of three phase induction motor with a neat diagram	II	L2	CO1	(8M)
	b) What is PMMC	II	L2	CO1	(2M)
5	a) Explain the hydal power plant with a neat diagram	III	L1	CO2	(8M)
	Explain current bill calculation	III	L2	CO3	(2M)
(OR)					
6	a) Explain the nuclear power plant with a neat diagram	III	L2	CO2	(8M)
	b) What are the precautionary methods to be taken to protect from electric shock	III	L1	CO2	(2M)
7	a) Define RMS value, Average value	I	L1	CO2	(5M)
	b) Find the equivalent resistance between A and B. 	I	L1	CO2	(5M)
(OR)					
8	a) Explain the working principle of alternator or generator	II	L2	CO3	(8M)
	b) Explain the fuse, MCB.	III	L3	CO2	(2M)

Answer